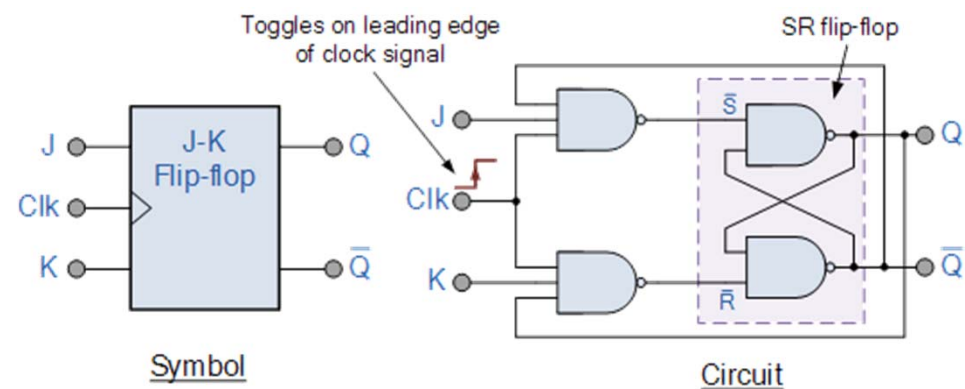



JK flip-flop

Truth Table

J	K	CLK	Q
0	0	↑	Q_0 (no change)
1	0	↑	1
0	1	↑	0
1	1	↑	$\bar{Q}_0$ (toggles)



JK master-slave flip-flop

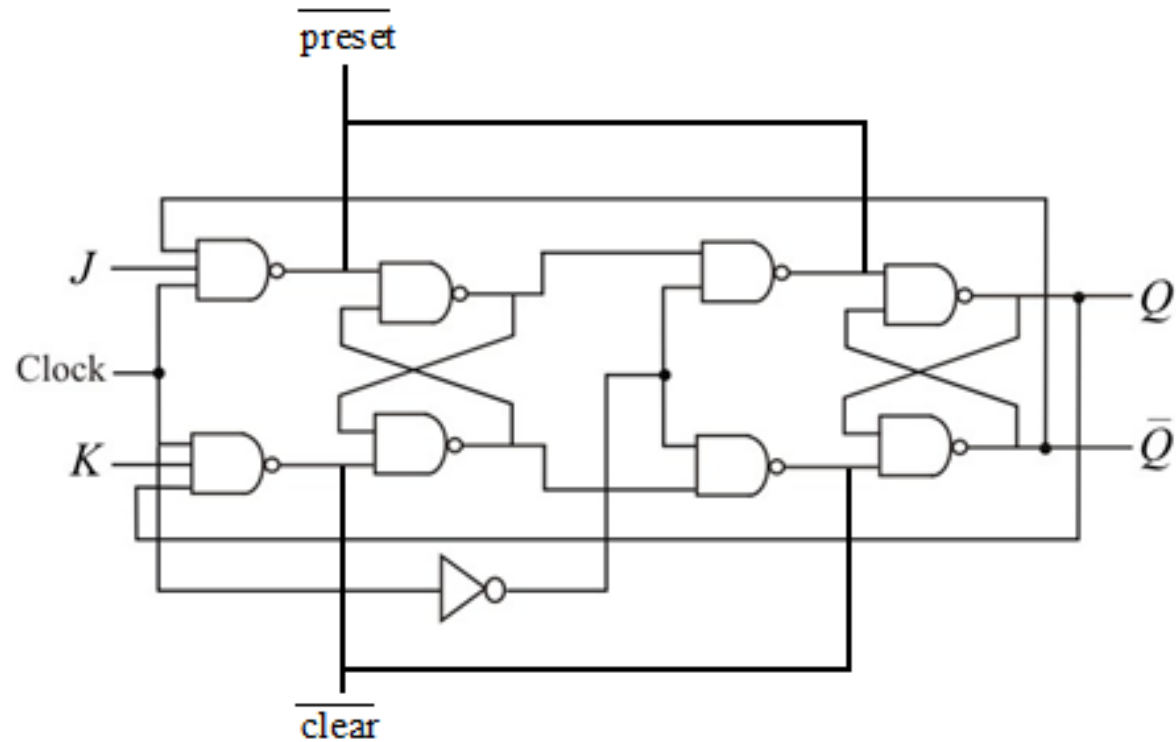

T flip-flop napravljen od JK flip-flopa

