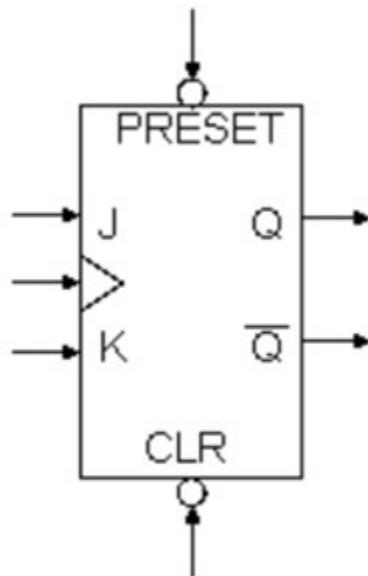


Vezba\_4\_JK\_FF

# Primer

Realizovati J-K flip-flop




Inputs				Outputs			
preset	clear	clk	J	K	Q	$\bar{Q}$	
0	X	X	X	X	1	0	
1	0	X	X	X	0	1	
1	1	no edge	X	X	Q	$\bar{Q}$	
1	1	↑	0	0	Q	$\bar{Q}$	
1	1	↑	1	0	1	0	
1	1	↑	0	1	0	1	
1	1	↑	1	1	toggle		

# Primer

```
module jk_flip_lfop(input clk, preset,clear,j,k, output q);
reg q=0;
always @(posedge clk or negedge preset or negedge clear)
begin
if(preset==0)
    q<=1'b1;
else
if (clear==0)
q<=1'b0;
else
case ({j,k})
2'b00 : q <= q; //ovaj red moze i da se izbrije
2'b01 : q <= 1'b0;
2'b10 : q <= 1'b1;
2'b11 : q <= ~q;
endcase
end
endmodule
```
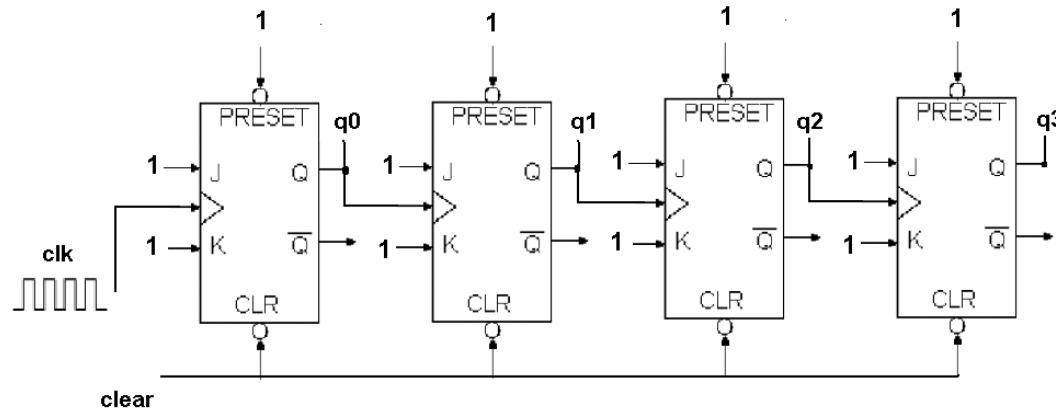
# Realizovati 4-bitni brojal uz pomoč J-K flip-fopova

```
module counter (input clk,preset,clear,j,k, output q0,q1,q2,q3);
jk_flip_lfop qq0 (.clk(clk), .preset(preset), .clear(clear), .j(j),.k(k), .q(q0));
jk_flip_lfop qq1 (.clk(q0), .preset(preset), .clear(clear), .j(j),.k(k), .q(q1));
jk_flip_lfop qq2 (.clk(q1), .preset(preset), .clear(clear), .j(j),.k(k), .q(q2));
jk_flip_lfop qq3 (.clk(q2), .preset(preset), .clear(clear), .j(j),.k(k), .q(q3));
Endmodule
```



```

module sim_counter;
    // Inputs
    reg clk;
    reg preset;
    reg clear;
    reg j;
    reg k;
    // Outputs
    wire q0;
    wire q1;
    wire q2;
    wire q3;


    // Instantiate the Unit Under Test (UUT)
    counter uut (
        .clk(clk),
        .preset(preset),
        .clear(clear),
        .j(j),
        .k(k),
        .q0(q0),
        .q1(q1),
        .q2(q2),
        .q3(q3)
    );

    initial begin
        // Initialize Inputs
        clk = 0;
        preset=0;
        clear=1;
        j=1;
        k=1;
        // Wait 100 ns for global reset to finish
        #100;
        // Add stimulus here
    end

    always @(*)
    begin
        #40;
        clk<=~clk;
    end

    always @(posedge clk)
    begin
        #100;
        preset<=1;
    end
endmodule

```

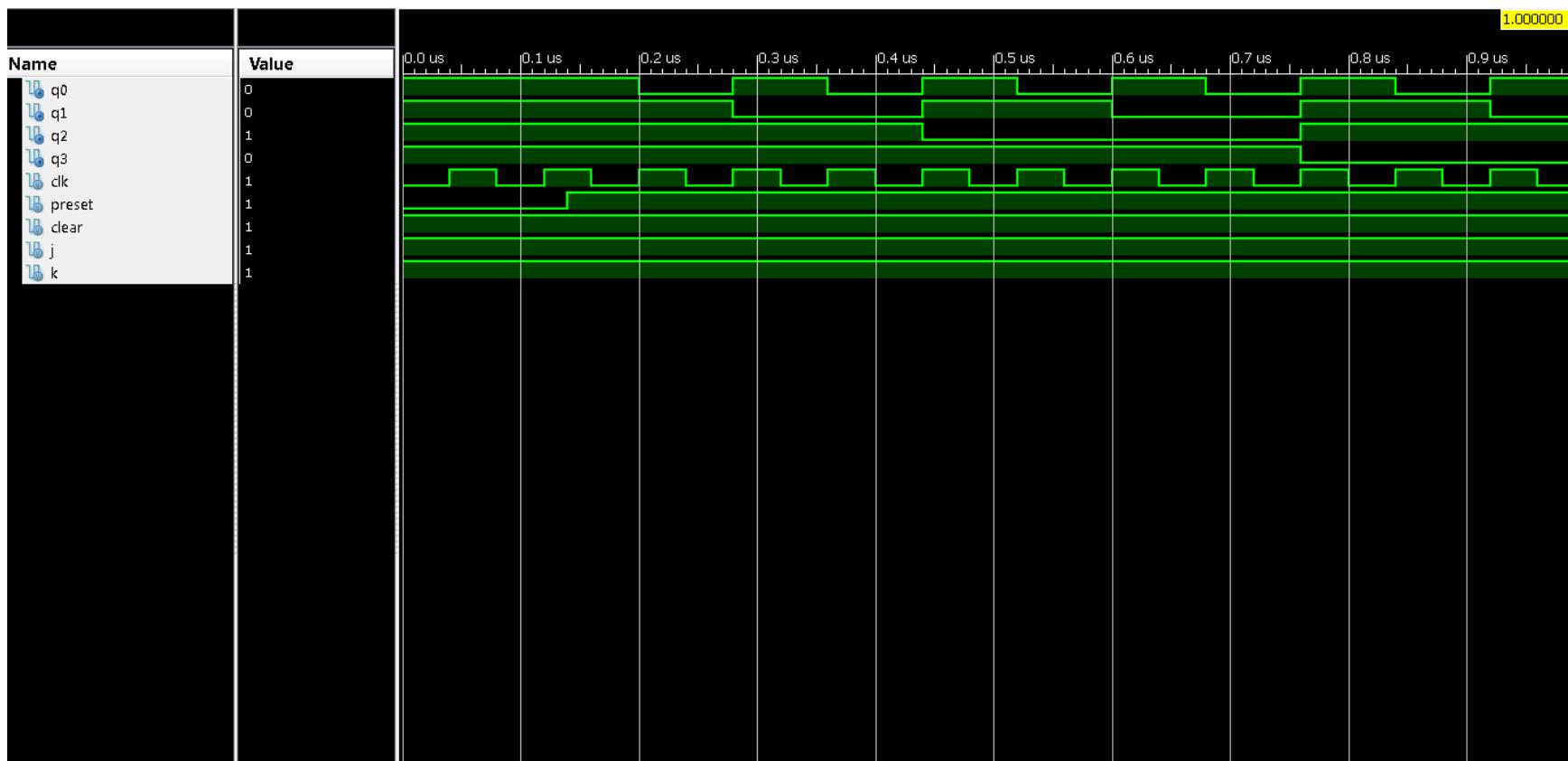

```
module counter (input clk, output q0,q1,q2,q3);
jk_flip lfop qq0 (.clk(clk),.q(q0));
jk_flip lfop qq1 (.clk(q0),.q(q1));
jk_flip lfop qq2 (.clk(q1),.q(q2));
jk_flip lfop qq3 (.clk(q2),.q(q3));
Endmodule
```

```
module jk_flip_ifop(input clk,output q);
reg q=0;
always @(posedge clk)
begin
q<=~q;
/*
if(preset==0)
q<=1'b1;
else
if (clear==0)
q<=1'b0;
else
case ({j,k})
2'b00 : q <= q; //ovaj red moze i da se izbrise
2'b01 : q <= 1'b0;
2'b10 : q <= 1'b1;
2'b11 : q <= ~q;
endcase */
end
endmodule
```

