

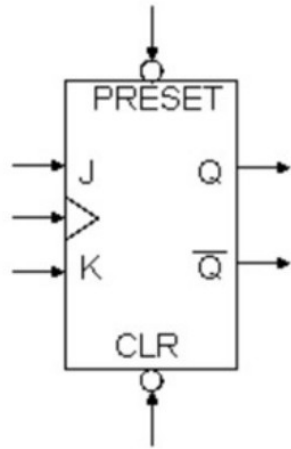


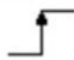

JK_FF_Brojac

Realizovati J-K flip-flop

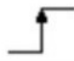

Inputs					Outputs	
preset	clear	clk	J	K	Q	\bar{Q}
0	X	X	X	X	1	0
1	0	X	X	X	0	1
1	1	no edge	X	X	Q	\bar{Q}
1	1		0	0	Q	\bar{Q}
1	1		1	0	1	0
1	1		0	1	0	1
1	1		1	1	toggle	

JK_FF_Brojac

